

UNIT I

Number Systems & Boolean Algebra

Binary arithmetic

GALGOTIAS
UNIVERSITY

BINARY ARITHMETIC

- The computer is a digital system that supports various arithmetic operations. It performs addition subtraction , multiplication and division over the binary dat.
- To learn the basic circuits of a digital system , it is necessary to study binary arithmetic operation such as binary addition , binary subtraction , binary multiplication and binary division .

1. Binary Addition

$0+0=0$, $0+1=1$, $1+0=1$, and $1+1=10$

example: 10110111

+ 01110101

Carry 1110111

100101100

2. Binary Subtraction

- The subtraction of two binary numbers is performed exactly in the same manner as the subtraction of decimal numbers.
- $0-0=0$, $0-1=-1$, $1-0=1$ and $1-1=0$
- $0-1=-1$ the result is negative it indicates that the second number is greater than the first one. Similar to decimal number system, a borrow is generated.

Example:

$$\begin{array}{r} 10100111 \\ - 01110101 \\ \hline 111 \quad \text{Borrow} \\ \hline 00110010 \end{array}$$

3. Binary Multiplication

- Its similar to the decimal multiplication . If the multiplier bits is 1, then the partial product is same as the multiplicand. If the multiplier bit is 0, then the partial product is 0.
- Example : $1010 * 1001$

$$\begin{array}{r} 1010 \text{ multiplicand} \\ 1001 \text{ multiplier} \\ \hline 1010 \\ 0000- \\ 0000-- \\ 1010--- \\ \hline 1011010 \end{array}$$

The binary division is same as the decimal division . Binary division has two results. i.e. quotient and remainder. Let us consider the example : 1011.11 is divided by 11

Basic Terminology

Gate : A device that performs a basic operation on electrical signals.

Boolean expressions: Uses Boolean algebra, a mathematical notation for expressing two-valued logic

Logic diagrams: A graphical representation of a circuit; each gate has its own symbol

Truth tables: A table showing all possible input value and the associated output values.

Six types of gates : NOT, AND, OR, XOR, NAND, NOR


NOT Gate

A NOT gate accepts one input signal (0 or 1) and returns the opposite signal as output.

Boolean Expression

$$X = A'$$

Logic Diagram Symbol

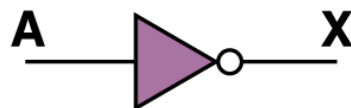

Truth Table

A	X
0	1
1	0


AND Gate

An AND gate accepts two input signals. If both are 1, the output is 1; otherwise, the output is 0

Boolean Expression

$$X = A \cdot B$$

Logic Diagram Symbol

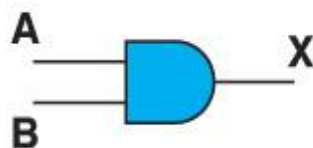

Truth Table

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1


OR Gate

An OR gate accepts two input signals. If both are 0, the output is 0; otherwise, the output is 1

Boolean Expression

$$X = A + B$$

Logic Diagram Symbol

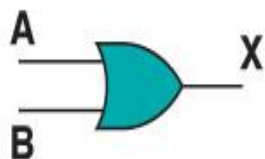


Truth Table

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

XOR Gate

An XOR gate accepts two input signals. If both are the same, the output is 0; otherwise, the output is 1

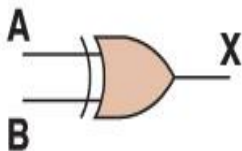Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = A \oplus B$		<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0
A	B	X															
0	0	0															
0	1	1															
1	0	1															
1	1	0															


NAND Gate

The NAND gate accepts two input signals. If both are 1, the output is 0; otherwise, the output is 1

Boolean Expression

$$X = (A \cdot B)'$$

Logic Diagram Symbol

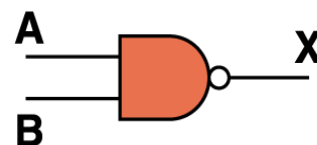

Truth Table

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0


NOR Gate

The NOR gate accepts two input signals. If both are 0, the output is 1; otherwise, the output is 0

Boolean Expression

$$X = (A + B)'$$

Logic Diagram Symbol

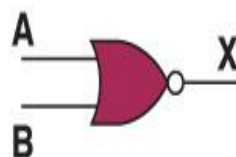

Truth Table

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0



Thank You