
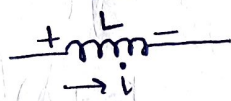
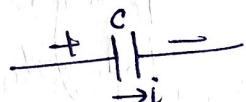
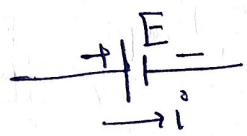


## Application of Linear Differential Equations to Electric Circuits

When a word problem converted into mathematical terms such as operators or expression then this is called Mathematical modeling.

Electric circuit made up of Voltage source which may be a battery or a generator and Resistance, inductance and capacitance.

Element	Symbol	
Charge	$q$	
Current	$i$	
Resistance	$R$	
Inductance	$L$	
Capacitance	$C$	
Emf or Voltage	$E$	

### Some laws:

(i)  $i = \frac{dq}{dt}$

(ii) Voltage drop across resistance  $= Ri$

(iii) " " inductance  $= L \frac{di}{dt}$

(iv) " " capacitance  $= \frac{q}{C}$

Kirchhoff's laws



(Emf)

Voltage law - The voltage impressed on a closed loop is equal to the sum of the voltage drops across all the other elements of the loop.

Current law - At any point of a circuit, the sum of the inflowing currents is equal to the sum of the outflowing currents.

~~Be~~ **Formulate** the physical system as a mathematical ~~model~~ expression in terms of variables, functions and equations and such an expression is known as a mathematical model of the problem.


The process of setting up a model, solving it mathematically and interpreting the result in physical or other terms is called mathematical modeling.

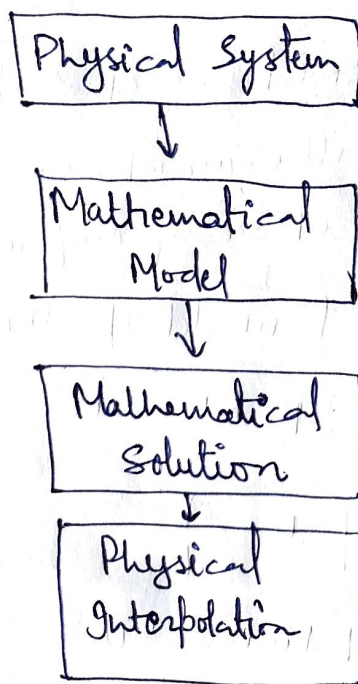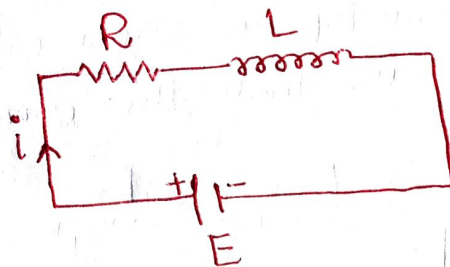Simple LR circuits

$$Ri + L \frac{di}{dt} = E$$

$$\Rightarrow \frac{di}{dt} + \frac{R}{L} i = \frac{E}{L}$$

## CR circuits

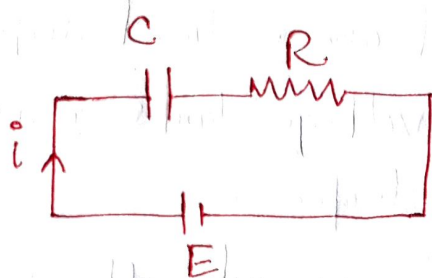


$$\frac{q}{C} + Ri = E$$

$$\Rightarrow R \frac{di}{dt} + \frac{1}{C} \frac{dq}{dt} = 0$$

$$\Rightarrow \frac{di}{dt} + \frac{1}{RC} i = 0$$


## LC circuits

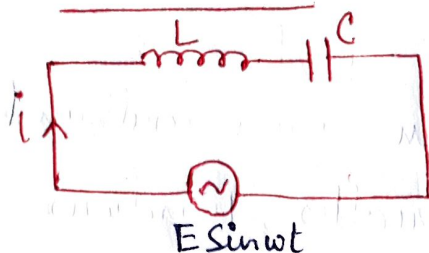

$$L \frac{di}{dt} + \frac{q}{C} = E \sin wt$$

$$\Rightarrow \frac{d^2 q}{dt^2} + \frac{1}{LC} q = E \sin wt$$

## LCR circuits

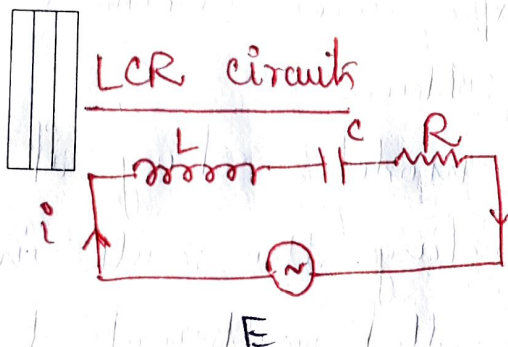


$$L \frac{di}{dt} + \frac{q}{C} + Ri = 0$$

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = 0$$

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

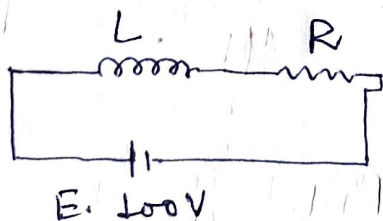Q. An inductance of 2 henry and a resistance of 20 ohms are connected in series with an EMF. If the current is zero when  $t=0$ , find the current at end of 0.01 sec if EMF is 100 volts.



Mathematical model of this circuit is

$$L \frac{di}{dt} + Ri = E$$

$$\Rightarrow \frac{di}{dt} + \frac{R}{L} i = \frac{E}{L}$$

$$\Rightarrow \frac{di}{dt} + 10 i = 50$$

Initial condition

$$i(0) = 0$$

$$i(0.01) = ?$$



This is a linear DE of order 1

$$I.f. = e^{+5t} = e^{10t}$$

Soln is  $i e^{10t} = \int 50 e^{10t} dt + A$

$$i e^{10t} = 5 e^{10t} + A$$

$$\Rightarrow i = 5 + A e^{-10t}$$

When  $t=0, i=0$

$$\Rightarrow 0 = 5 + A e^0 \Rightarrow A = -5$$

$$\therefore i = 5(1 - e^{-10t})$$

Now,  $t = 0.01$  then

$$i = 5(1 - e^{-10 \times 0.01}) = 5(1 - e^{-0.1})$$

$$= 5(1 - e^{-0.1})$$

Q. A 20 ohms resistor is connected in series with a capacitor of 0.01 farad and emf  $E = 40e^{-3t} + 20e^{-6t}$ . If  $q=0$  at  $t=0$ , find charge at time  $t$ .

By Voltage law

$$Ri + \frac{q}{C} = E$$

$$\Rightarrow \frac{dq}{dt} + \frac{1}{RC} q = \frac{E}{R}$$

$$\Rightarrow \frac{dq}{dt} + 5q = \frac{1}{20} (40e^{-3t} + 20e^{-6t})$$

$$\therefore \frac{dq}{dt} + 5q = 2e^{-3t} + e^{-6t}$$

$$\therefore I.f. = e^{+5t}$$

Soln is

$$q e^{5t} = \int e^{5t} (2e^{-3t} + e^{-6t}) dt + A$$

$$= 2 \int e^{2t} dt + \int e^{-t} dt + A$$

$$= e^{2t} - e^{-t} + A$$

$$\therefore q = e^{-3t} - e^{-6t} + A e^{-5t}$$

When  $t=0, q=0$

$$\Rightarrow A=0$$

$$\therefore \boxed{q(t) = e^{-3t} - e^{-5t}}$$

L22.

Q. Find current when  $L = 0.5 \text{ H}$ ,  $C = 0.005 \text{ F}$ , and  $E = \sin t \text{ V}$ , assuming zero initial current and charge.

By Voltage law,

$$L \frac{di}{dt} + \frac{q}{C} = E$$

$$\Rightarrow \frac{d^2 i}{dt^2} + \frac{1}{LC} i = \frac{1}{L} E'$$

$$\Rightarrow \frac{d^2 i}{dt^2} + 400 i = 2 \cos t$$

$$C.F. = m^2 + 400 = 0 \Rightarrow m^2 = -400 \Rightarrow m = \pm 20i$$

$$i_h(t) = A \cos 20t + B \sin 20t$$

$$i_p(t) = \frac{2}{D^2 + 400} \cos t = \frac{2}{399} \cos t$$

$$\therefore i(t) = A \cos 20t + B \sin 20t + \frac{2}{399} \cos t$$

$$\text{When } i=0, t=0 \Rightarrow 0 = A + \frac{2}{399} \Rightarrow A = -\frac{2}{399}$$

$$\text{And } \frac{dq}{dt} = A \cos 20t + B \sin 20t + \frac{2}{399} \cos t$$

$$q(t) = \frac{A}{20} \sin 20t - \frac{B}{20} \cos 20t + \frac{2}{399} \sin t$$

$$\text{When } t=0, q=0 \Rightarrow 0 = -\frac{B}{20} \Rightarrow B = 0$$

$$\therefore \boxed{i(t) = \frac{2}{399} (\cos t - \cos 20t)}$$